

## BUILD A Stop Light

### WHAT YOU'LL LEARN

LED stands for "Light Emitting Diode." The LED only lets the current go in one direction. The LED piece is like the wire except it has a part of it missing in the middle. When the current gets to the hole, it jumps across. When it jumps, it gives off light.

### WHAT YOU'LL NEED



1-POINT WIRE (x2)



4-POINT WIRE (x2)



GREEN LED (x1)



YELLOW LED (x1)



RED LED (x1)



BATTERY (x1)




Magnetic, snap-together modules  
for learning basic circuitry

BUILD A

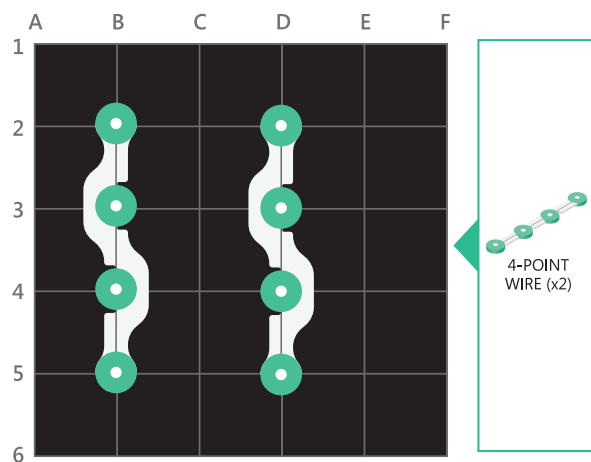
# Stop Light




Magnetic, snap-together modules  
for learning basic circuitry



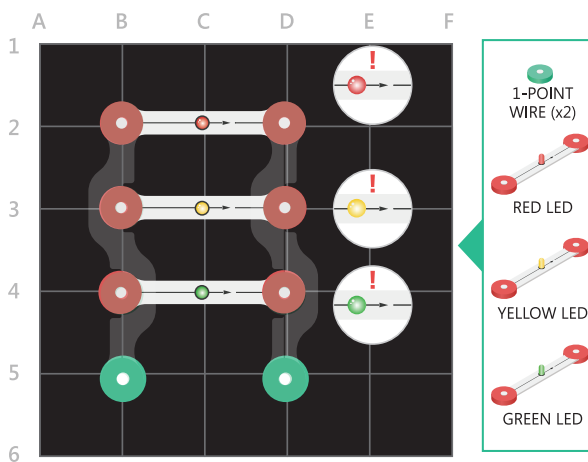**Step 1:** Place two 4-point wire components on the board as shown



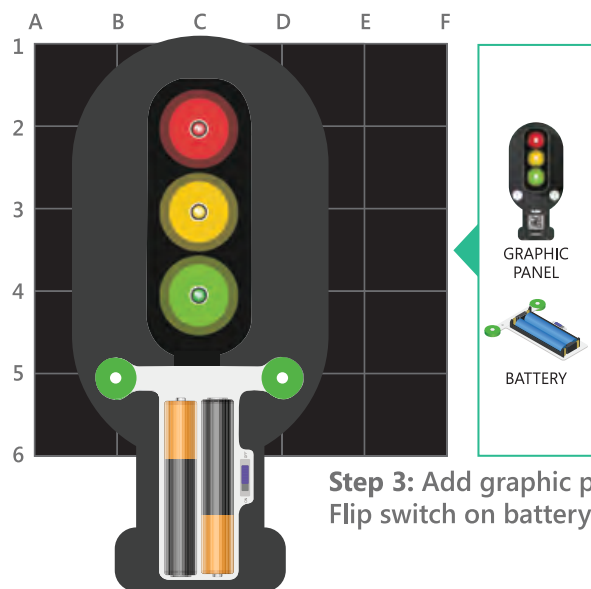**Step 2:** Place the red LED, yellow LED, and green LED on the board as shown. Place two 1-point wire components on the two remaining open points.



**Step 3:** Add graphic panel and battery. Flip switch on battery to "ON" position.

